

KATHMANDU UNIVERSITY  
End Semester Examination  
February/March, 2018

Marks Scored:

Level: B. E.

Year : II

Exam Roll No. :

Time: 30 mins.

Course : EEEG 204

Semester : I

F. M. : 20

Registration No.:

Date : MAR 06 2018

SECTION "A"

[20 Q. × 1 = 20 marks]

Choose the most appropriate answer.

1. Valence electrons are \_\_\_\_\_.  
a. in the closest orbit to the nucleus      b. in various orbits around the nucleus  
c. in the most distant orbit from the nucleus      d. not associated with a particular atom
2. A trivalent impurity is added to silicon to create \_\_\_\_\_.  
a. germanium      b. a n-type semiconductor  
c. a depletion region      d. a p-type semiconductor
3. If the load resistance of a capacitor filtered full wave rectifier is reduced, the ripple voltage \_\_\_\_\_.  
a. is not affected      b. increases  
c. decreases      d. has different frequency
4. A 12 V zener diode has zener current variation of 10 mA which produces a 0.1 V change in zener voltage. The zener impedance for this current range is \_\_\_\_\_.  
a. 0.1  $\Omega$       b. 100  $\Omega$       c. 10  $\Omega$       d. 1  $\Omega$
5. For operation as an amplifier, the base of a npn transistor must be \_\_\_\_\_.  
a. 0 V      b. negative with respect to the emitter  
c. 5 V      d. positive with respect to the emitter
6. If  $I_C$  is 50 times larger than  $I_B$ , then  $\beta_{DC}$  is \_\_\_\_\_.  
a. 500      b. 0.02      c. 100      d. 50
7. In saturation mode of operation of transistor,  $V_{CE}$  is \_\_\_\_\_.  
a. 0.7 V      b. equal to  $V_{CC}$       c. maximum      d. minimum
8. A JFET always operates with \_\_\_\_\_.  
a. the gate to source pn junction forward biased  
b. the gate connected to the source  
c. the gate to source pn junction reverse biased  
d. the drain connected to ground
9. If the input to the circuit of figure 1 is a sine wave, the output will be \_\_\_\_\_.  
a. half wave rectified sine wave  
b. full-wave rectified sine wave  
c. triangular wave  
d. square wave

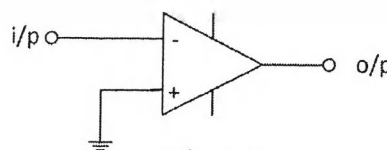


Figure 1



KATHMANDU UNIVERSITY  
End Semester Examination  
February/March, 2018

MAR 06 2018

Level : B. E.  
Year : II  
Time : 2 hrs. 30 mins.

Course : EEEG 204  
Semester : I  
F. M. : 55

SECTION "B"

Attempt *ANY FIVE* questions. Missing data may be suitably assumed. Each symbol carries their usual meaning.

1. a. What is a *pn* junction? How is the electric field across the *pn* junction created? Explain with the help of suitable sketch. [3]
- b. What factors must be included to more accurately represent a diode? Explain with the help of suitable example. [4]
- c. The following characteristics are specified for a particular Zener diode:  $V_Z = 29\text{ V}$ ,  $V_R = 16.8\text{ V}$ ,  $I_{ZT} = 10\text{ mA}$ ,  $I_R = 20\text{ }\mu\text{A}$ , and  $I_{ZM} = 40\text{ mA}$ . Sketch the characteristic curve showing all the given values; also explain the significance of major parameters. [2+2]
  
2. a. Determine  $I$ ,  $V_1$ ,  $V_2$ , and  $V_o$  for the circuit shown in Figure 1. [6]
- b. Explain the working mechanism of energy meter with suitable diagram. [5]

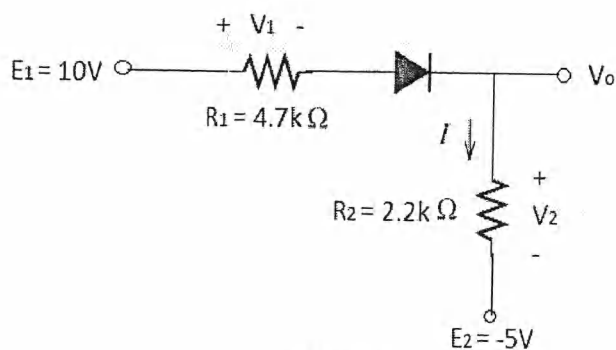


Figure 1

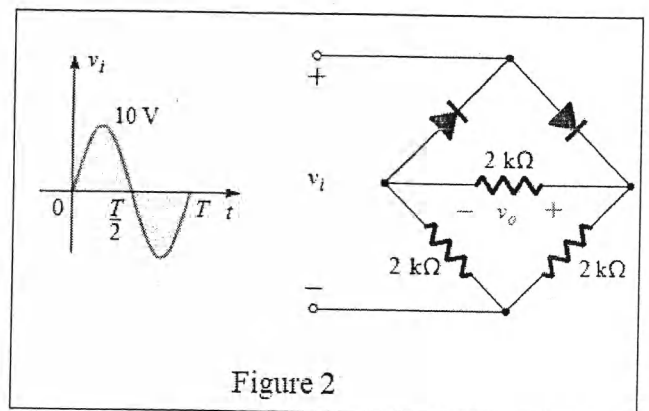


Figure 2

3. a. Determine the output waveform for the network shown in Figure 2, and calculate the output dc level and the required PIV of each diode. [4]
- b. What are the static characteristics of measuring devices? Explain the working principle of LVDT and moving iron instruments. [2+5]
  
4. a. Sketch an ideal family of collector curves for the circuit shown in Figure 3 for  $I_B = 5\text{ mA}$  to  $25\text{ mA}$  in  $5\text{ mA}$  increments. Assume  $\beta_{DC} = 100$  and that  $V_{CE}$  does not exceed breakdown. [4]
- b. Determine whether or not the transistor shown in Figure 4 is in saturation. [4]  
Assume  $V_{CE(sat)} = 0.2\text{ V}$ .
- c. Differentiate between JFET and MOSFET. [3]

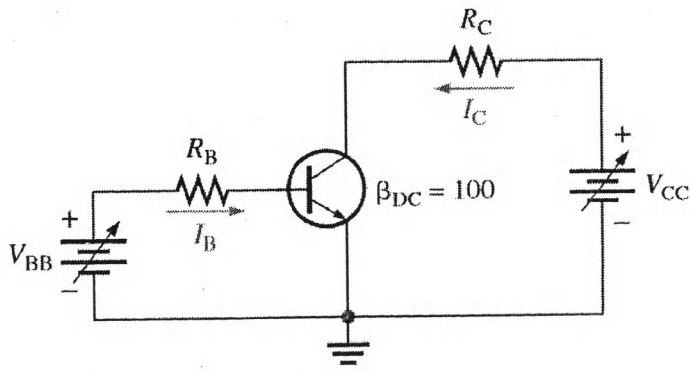


Figure 3

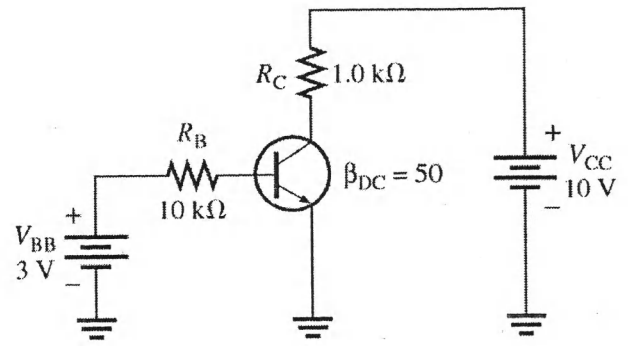


Figure 4

5. a. Explain the types, symbol, characteristics and applications of thyristors. [5]
- b. Explain the working principle of summing amplifier. Derive the output expression for the summing amplifier used to sum 5 different input values. [6]
  
6. a. Differentiate R to 2 R ladder and Binary weighted digital to analog converter. [4]
- b. Sketch and explain the working of circuit which convert analog signal in to 4 digit digital signal. [4]
- c. Differentiate between thermocouple and thermistor. [3]